

Unit 8

Saturday, March 20, 2021 9:06 PM

I. Chapter 16

- a. Static Electricity; Electric Charge and Its Conversion
 - i. Unlike charges attract; like charges repel
 - ii. Law of conservation of electric charge
 - 1) The net amount of electric charge produced in any process is zero
 - 2) No net electric charge can be created or destroyed
- b. Induced Charge; the Electroscope
 - i. Charging by conduction: Where electrons get transferred and objects end up with the sign of charge
- c. Coulomb's Law: $F = k \frac{q_1 q_2}{r^2}$
 - i. $k = 8.98 \times 10^9 \text{ Nm}^2 / \text{C}^2$

II. Electric Currents

- a. Electric Current
 - i. Circuit: When a continuous conducting path is connected between the terminals of a battery
 - ii. Electric Current: A flow of charge
 - iii. Ampere: Current, measured in coulombs per second
 - iv. Complete Circuit: A circuit with a continuous conducting path
 - v. Open Circuit: When no current flows
- b. Ohm's Law: Resistance and Resistors
 - i. Ohm's Law: $V = IR$
 - ii. Graphs
 - 1) $f(V) = I; \frac{\Delta I}{\Delta V} = \frac{1}{R}$
 - iii. Voltage Drop/Potential Drop: An electric potential decrease
 - iv. Resistivity of wires: $R = \frac{\rho L}{A}$
- c. Electric Power:
 - i. Power: $P = IV$
 - ii. Watt: $1W = 1 \left(\frac{J}{s} \right)$

III. DC Circuits

- a. EMF and Terminal Voltage
 - i. Electromotive force: Converts other forms of energy to electric
 - ii. Internal Resistance: The resistance in the power source
 - iii. Terminal Voltage: $V_{+} = \mathcal{E} - V_{+}$
- b. Resistance in Series and in Parallel
 - i. Series Circuits
 - 1) Properties
 - a) $I_s = I_1 = I_2 = I_3 = I_4 = I_5 = I_6 = I_7 = I_8 = I_9 = I_{10}$
 - b) $R_s = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7 + R_8 + R_9 + R_{10}$
 - c) $V = V_1 + V_2 + V_3 + V_4 + V_5 + V_6 + V_7 + V_8 + V_9 + V_{10}$
 - d) Ohm's Law Applied: $V_s = I_s R_s = I_s (R_1 + R_2 + \dots)$
 - 2) Changes to circuit

Net Change	Voltage	Resistance	Current
Voltage Increase	Increase	Constant	Increase
Voltage Decrease	Decrease	Constant	Decrease
Resistor Added	Constant	Increase	Decrease
Resistor Removed	Constant	Decrease	Increase
Current Increase	Increase	Constant	Increase
Current Decrease	Decrease	Constant	Decrease

ii. Parallel

- 1) Properties
 - a) $I_s = I_1 + I_2 + I_3 + I_4 + I_5 + I_6 + I_7 + I_8 + I_9 + I_{10}$
 - b) $V_s = V_1 = V_2 = V_3 = V_4 = V_5 = V_6 = V_7 = V_8 = V_9 = V_{10}$
 - c) $\frac{1}{R_s} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_7} + \frac{1}{R_8} + \frac{1}{R_9} + \frac{1}{R_{10}}$
- 2) Changes to circuit

Net Change	Voltage	Resistance	Current
Voltage Increase	Increase	Constant	Increase
Voltage Decrease	Decrease	Constant	Decrease
Resistor Added	Constant	Decreases	Increase
Resistor Removed	Constant	Increase	Decrease
Current Increase	Increase	Constant	Increase
Current Decrease	Decrease	Constant	Decrease

iii. Common Examples: Series + Parallel as Bulbs

- 1) Description: R_s series to $R_1, R_2,$ and R_3 as parallel
- 2) Changes

	R_s	R_1	R_2	R_3
No Change	Brightest	Lowest	Lowest	Lowest
R_s Increase	Dimmer	Dimmer	Dimmer	Dimmer
R_1 Increase	Dimmer	Increase	Increase	Increase
R_1 Decrease	Increase	Dimmer	Dimmer	Dimmer

c. Kirchhoff's Rules

- i. Junction (1st) Rule: At any junction point, the sum of all currents entering the junction must equal the sum of all currents leaving the junction
- ii. Loop (2nd) Rule: The sum of the changes in potential around any closed path of a circuit must be zero
- iii. Solving common problems for direction and magnitude:
 - 1) Using the junction rule, we can determine that at a specific junction, the sum of inputs must equal the output. Example: $I_1 + I_2 = I_3$
 - 2) Using the loop rule (positive to negative), generate equations with $V - I R = 0$, current with the opposite directions are negative (ie add instead of subtract)
 - 3) Solve as a system of equations, if a current is negative, reverse the direction

d. Brightness

- i. Brightness is determined by power

$$P = IV = I^2 R = \frac{V^2}{R}$$